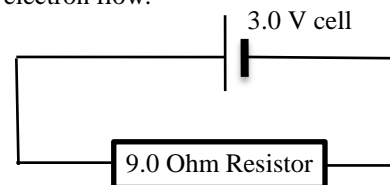


05 Electric currents review questions


1. Simple circuit.

Look at the circuit on the right

- Draw arrows showing the direction of the current flow and the direction of the electron flow.
- State the value of the potential difference across the 9.0 Ohm resistor.
- Calculate the current flowing through the circuit.
- Calculate the power dissipated in the resistor.
- How long would it take before 60 Joules of energy had been transferred?
- How many coulombs of charge will have flowed in this time?
- How many electrons will have flowed through the resistor in this time?



2. In line (series) circuit.

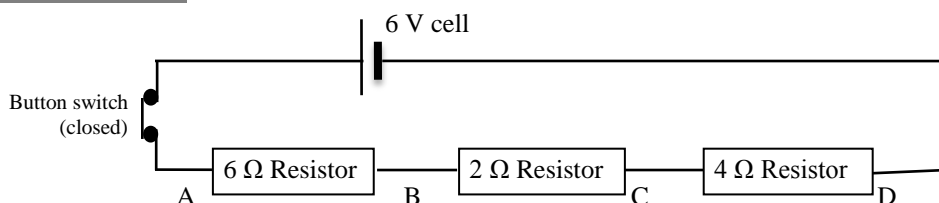


- Calculate the total resistance of the circuit.
- Calculate the current flowing around the circuit.
- Calculate the potential differences between:
 - A and B
 - B and C
 - C and D
 - A and C
 - A and D
- Calculate the power being dissipated at each of the loads

3. Parallel circuit

- Redraw the circuit as a parallel circuit with a button switch for each load. Explain what the advantages of parallel circuits are.
- Calculate the combined resistance of the three parallel loads and hence the total current.
- Show that this total current is consistent with calculating the current through each of the three resistors independently and adding the result.

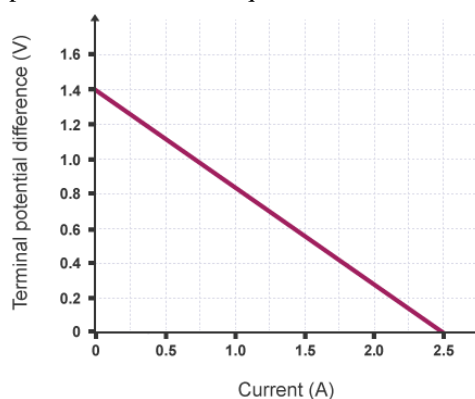4. Additional circuit bits.

- In questions 2 which resistor has the most power dissipated across it and in questions 3 which resistor has the most power dissipated across it?
- The 6V cell will in reality has internal resistance. The internal resistance is 1 Ohm .
 - What is the current flowing?
 - What is the potential difference at the cell terminals?
- Measuring the values of current and resistance will also affect the values. Explain this statement.
- The graph shows measurements of potential difference at the terminal of a cell varying with current. Calculate the internal resistance of the cell.



5. Resistivity and Ohms law

- A wire of diameter 0.5mm and length 0.8m has a resistance of 8 Ohms. Calculate the resistivity of the wire.
- Potential difference does not affect resistivity but if the temperature of the wire increases the resistivity of the wire increases. Explain whether or not the wire obeys Ohm's law.
- Sketch a graph of Current against voltage for a perfect resistor, this wire and a filament lamp.

6. Drift speed

A copper wire of 1mm cross-sectional area has 1A of current flowing through it. The density of copper is 8900 kgm^{-3} and atomic mass no. 63.5u. What is the average drift velocity of electrons assuming one free electron per copper atom?


7. Magnetic effects

(a) Draw the magnetic field pattern produced by:

- i) a long, straight current carrying wire
- ii) a bar magnet
- iii) solenoid


(b) The 0.1m wire in the diagram opposite is carrying a current of 2.0A; the field strength is 0.024 Tesla, $\phi=45^\circ$.

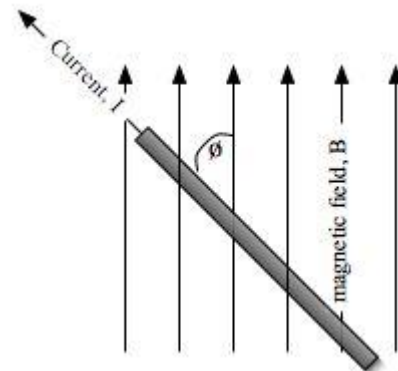- i) In what direction is the force on the wire?
- ii) What is the magnitude of this force?
- iii) If an alpha particle is travelling in the same direction as the current at 5% of the speed of light what is the force acting on it?



(c) Look at the diagram opposite

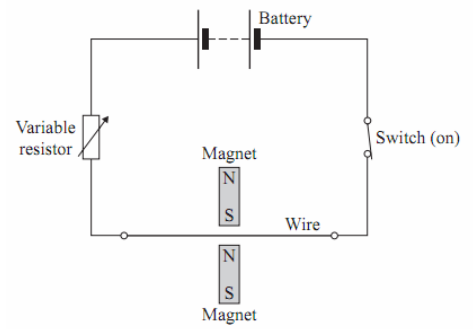- i) Determine the direction of the force on the wire due to the interaction of its magnetic field and the magnets.
- ii) If the field strength in between the magnets is 0.2T and approximately 0.1m of wire is affected by the field calculate the size of the force.



8. Coulombs law

- (a) State Coulombs law.
- (b) Two paint droplets are charge with +0.5mC. If they are 1mm apart what force is acting between them (assuming the electric permittivity of air is 1.0)?
- (c) If the droplets are between a positively charged plate and a negatively charged car door there is a force of 0.4N acting on the droplets. Calculate the field strength in between the plates.
- (d) If the work done accelerating the droplet onto the car door is 0.1J what voltage has the droplet moved through?
- (e) If the droplets in (b) are within a block of polyethylene which has a permittivity of 2.2 what will the force be?