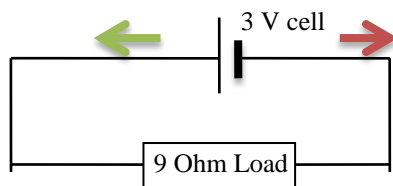



## 05 Electric currents review answers

### 1. Simple circuit.



- (a) Draw the circuit.
- (b) Draw arrows showing the direction of the **current flow** and the direction of the **electron flow**.
- (c) State the value of the potential difference across the 9 Ohm load. **V = 3 Volts**
- (d) Calculate the current flowing through the circuit. **I = V/R = 0.33A**
- (e) By considering the definition of potential difference and that current is a flow rate of charge explain why the power dissipated in the resistor is equal to 1 Watts.  
**p.d. = energy per unit charge and current is charge per unit time so**  
**p.d. x current = energy per unit time = 3 x 0.33 = 1Watt**
- (f) Derive a formula for power dissipated based on the values of current and resistance only.  
**P = VI and V = IR so by substitution P = IxRxI = I<sup>2</sup>R.**
- (g) How long would it take before 60 Joules of energy had been transferred to the load from the cell?  
**1 Watt = 1 Joule per second.....60 seconds**
- (h) How much energy does each individual electron supply to the load?  
 i) in eV 1eV is the energy gained when 1 electron accelerates over one volt. **3eV**  
 ii) in Joules **1e = 1.6x10<sup>-19</sup>C 3eV = 3x1.6x10<sup>-19</sup> = 4.8x10<sup>-19</sup> Joules**
- (g) How many electrons will have flowed through the resistor to transfer the 60 Joules of energy?  
**0.33 coulombs per second x 60 seconds ÷ 1.6 x 10<sup>-19</sup>C =**  
**Easier..... 60 ÷ 4.8x10<sup>-19</sup> = 1.25x10<sup>20</sup>**

### 2. In line (series) circuit.

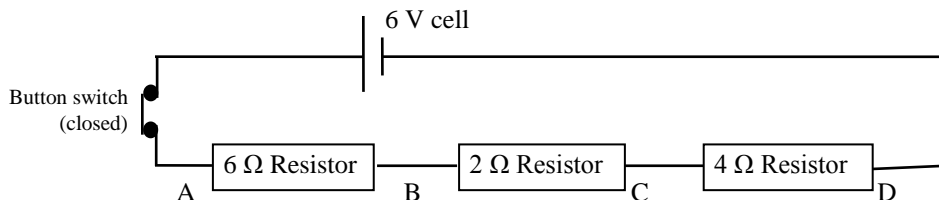

- (a) Calculate the total resistance of the circuit. **12 Ω**
- (b) Calculate the current flowing around the circuit. **0.5A**
- (c) Calculate the potential differences between:  
 (i) A and B **3V** (ii) B and C **1V** (iii) C and D **2V** (iv) A and C **4V** (v) A and D **6V**
- (d) Calculate the power being dissipated at each of the loads **A: 1.5W, B: 0.5W, C: 1W, D: 3W**

### 3. Parallel circuit

- (a) Redraw the circuit as a parallel circuit with a button switch for each load. Explain what the advantages of parallel circuits are. Each component receives the supply voltage and can be switch on/off independently.
- (b) Calculate the combined resistance of the three parallel loads and hence the total current.  
**1/R = 1/6 + 1/2 + 1/4 = 2/12 + 6/12 + 3/12 = 11/12 so R = 12/11 = 1.09 Ω**  
**I = 6/1.09 = 5.5 A**
- (c) Show that this total current is consistent with calculating the current through each of the three resistors independently and adding the result.  
**6 Ω : I = 6/6 = 1A, 2 Ω: I=6/2 = 3A, 4 Ω: I=6/4 = 1.5A These sum to 5.5A**

### 4. Additional observations.

- (a) In questions 2 which resistor has the most power dissipated across it and in questions 3 which resistor has the most power dissipated across it. **Most power in series is the highest value resistor (P=I<sup>2</sup>R, I is the same for all resistors, Most power in parallel is lowest value resistor (P=V<sup>2</sup>/R)**

- (b) Measuring the values of current and resistance will affect the values. Explain this statement. **Voltmeters do not have infinite resistance and ammeters do not have zero resistance so they will affect the current flow.**
- (c) The 6V cell in questions 3 and 4 will in reality have internal resistance. Will this affect the answers to question 3 or 4 the most? **This will affect the answers to 4 the most as  $V_s = V_{emf} - Ir$  and  $I$  is higher in 4.**


**5. Resistivity and Ohms law**

(a) A wire of diameter 0.5mm and length 0.8m has a resistance of 8 Ohms. Calculate the resistivity of the wire.

**$R = \rho L/A$  so  $\rho = RA/L = 8 \times 2\pi(0.5 \times 10^{-3}/2)^2/0.8 = 3.9 \times 10^{-6} \Omega m$**

(b) Potential difference does not affect resistivity but if the temperature of the wire increases the resistivity of the wire increases. Explain whether or not the wire obeys Ohm's law. **The wire does obey Ohms law if resistivity does not change.**

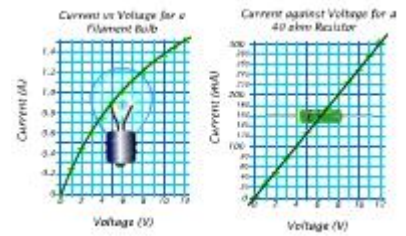(c) Sketch a graph of Current against voltage for a perfect resistor, this wire and a filament lamp.



**6. Specialized circuits**

(a) The circuit opposite is used to control a lighting circuit. In the day time the LDR has a resistance of 200Ω. At night the LDR has a resistance of 5000Ω. The lighting system needs at least 8 V to operate. Show that the lighting circuit will be activated in the night but not in the day.

**Day:**


**$R_{total} = 1200 \Omega$  so  $I = 12/1200 = 0.01A$**

**$V$  across LDR =  $0.01 \times 200 = 2V$  (lighting system off)**


**Day:**

**$R_{total} = 6000 \Omega$  so  $I = 12/6000 = 0.002A$**

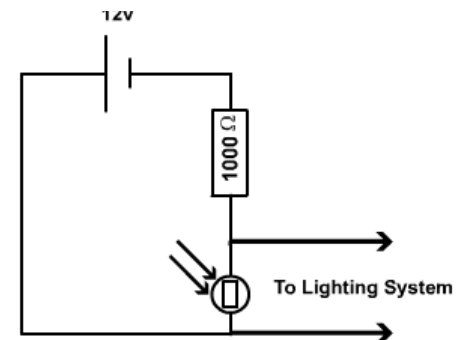**$V$  across LDR =  $0.002 \times 5000 = 10V$  (lighting system on)**



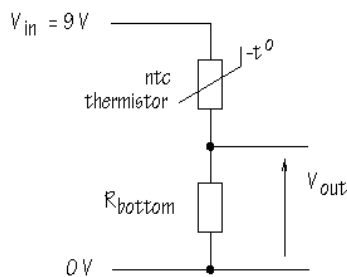(b) A similar circuit shown below can be used to control a heating system using a NTC thermistor.



**In this circuit when it is cold resistance of the thermistor is high.**

**(i) At cold temperature a higher proportion of the 9V P.D. will be across the thermistor so  $V_{out}$  will be low.**

**The heating system therefore activates at low  $V_{out}$  P.D.**

**(ii)  $R_{total} = 220k\Omega$**

**$I = V/R = 9/220k$**

**$V_{out} = IR = (9/220k) \times 100k = 4.1V$**

The system should activate when it is cold. Explain whether the heating system will be activated by a low or high potential difference at  $V_{out}$ .

(c) In the strain gauge circuit below  $R_1$ ,  $R_2$ ,  $R_3$  and the strain gauge all have the same resistance when the gauge is not under strain. A very sensitive Voltmeter can therefore be used as the voltage measured is always small. If the strain gauge resistance increases slightly which side of the voltmeter will have a positive voltage compared to the other side? **Strain gauge p.d. will increase so RHS will be positive.**

