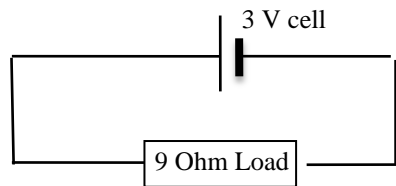



05 Electric currents review questions

1. Simple circuit.



- Draw the circuit.
- Draw arrows showing the direction of the current flow and the direction of the electron flow.
- State the value of the potential difference across the 9 Ohm load.
- Calculate the current flowing through the circuit.
- By considering the definition of potential difference and that current is a flow rate of charge explain why the power dissipated in the resistor is equal to **1 Watt**.
- Derive a formula for power dissipated based on the values of current and resistance only.
- How long would it take before 60 Joules of energy had been transferred to the load from the cell?
- How much energy does each individual electron supply to the load?
 - in eV
 - in Joules
- How many electrons will have flowed through the resistor to transfer the 60 Joules of energy?

2. In line (series) circuit.

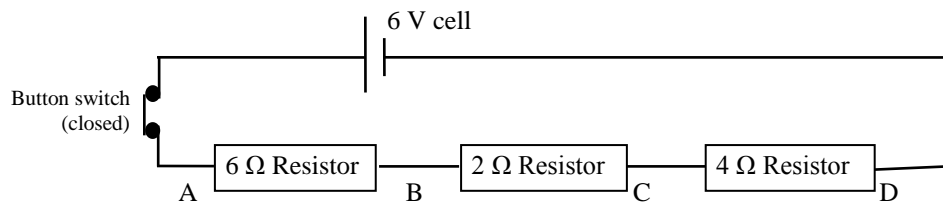

- Calculate the total resistance of the circuit.
- Calculate the current flowing around the circuit.
- Calculate the potential differences between:
 - A and B
 - B and C
 - C and D
 - A and C
 - A and D
- Calculate the power being dissipated at each of the loads

3. Parallel circuit

- Redraw the circuit as a parallel circuit with a button switch for each load. Explain what the advantages of parallel circuits are.
- Calculate the combined resistance of the three parallel loads and hence the total current.
- Show that this total current is consistent with calculating the current through each of the three resistors independently and adding the result.

4. Additional observations.

- In questions 2 which resistor has the most power dissipated across it and in questions 3 which resistor has the most power dissipated across it.
- Measuring the values of current and resistance will affect the values. Explain this statement.
- The 6V cell in questions 3 and 4 will in reality have internal resistance. Will this affect the answers to question 3 or 4 the most?

5. Resistivity and Ohms law

- A wire of diameter 0.5mm and length 0.8m has a resistance of 8 Ohms. Calculate the resistivity of the wire.
- Potential difference does not affect resistivity but if the temperature of the wire increases the resistivity of the wire increases. Explain whether or not the wire obeys Ohm's law.
- Sketch a graph of Current against voltage for a perfect resistor, this wire and a filament lamp.


6. Specialized circuits

(a) The circuit opposite is used to control a lighting circuit.

In the day time the LDR has a resistance of 200Ω . At night the LDR has a resistance of 5000Ω . The lighting system needs at least 8 V to operate.

Show that the lighting circuit will be activated in the night but not in the day.

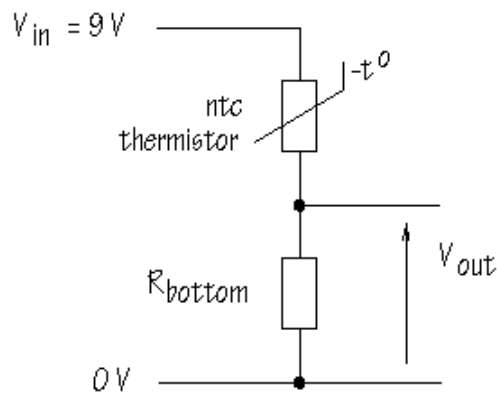(b) A similar circuit shown below can be used to control a heating system using a NTC thermistor.



The system should activate when it is cold.

- (i) Explain whether the heating system will be activated by a low or high potential difference at V_{out} .
- (ii) Calculate V_{out} if $R_{bottom} = 100k\Omega$ and thermistor resistance = $120k\Omega$.

(c) In the strain gauge circuit below R_1 , R_2 , R_3 and the strain gauge all have the same resistance when the gauge is not under strain. A very sensitive Voltmeter can therefore be used as the voltage measured is always small. If the strain gauge resistance increases slightly which side of the voltmeter will have a positive voltage compared to the other side?

Quarter-bridge strain gauge circuit

